

DIGITAL ELECTRONICS
3rd Exam/ECE/CSE/IT/0195/Nov'24
(For 2018 Batch onwards)

Duration: 3Hrs.

M.Marks:75

SECTION-A

15x1=15

Q1. Do as directed.

- a. Define Digital Signal.
- b. The decimal number equivalent to $(1101)_2$ is _____
- c. How many digits in octal system?
- d. The 2's complement of 11001000 is _____
- e. BCD stands for _____.
- f. How many numbers of characters represented by ASC-II CODE?
- g. The hexadecimal digits are 0 to 9 and A to _____
- h. A ripple counter is _____ Sequential circuit.
- i. The modulo of a 4-bit binary counter is _____
- j. BCD numbers express each decimal digit as a _____
- k. Pocket calculators use _____ system.
- l. An inverter is also known as _____ gate.
- m. Full subtractor has how many outputs?
- n. A half subtractor subtracts how many bits?
- o. IC 74194 is which shift register?

SECTION-B

6x5=30

Q2. Attempt any six questions.

- i. List out differences between an Analog and Digital signal.
- ii. Draw and write the truth table of OR gate.
- iii. State and verify Duality principle.
- iv. What do you mean by minterm and maxterm?
- v. What do you mean by SOP and POS.?
- vi. Differentiate between combinational and sequential circuits.
- vii. Design and implement a half subtractor.
- viii. What are the basic differences between MUX and DEMUX?
- ix. Give applications of flip-flops.
- x. Discuss the working of buffer register.

SECTION-C

3x10=30

Q3. Attempt any three questions.

- a. Define and explain universal shift register in detail.
- b. What do you mean by ripple counter explain?
- c. What is race around condition in JK flip flop? How can it be avoided?
- d. Design 4:1 multiplexer.
- e. Prove the following logic expression using Boolean algebra:
 $AB+CD = (A+C)(A+D)(B+C)(B+D)$

P.S.B.T.E. & I.T.