

**DIGITAL ELECTRONICS**  
**3<sup>rd</sup> Exam/ECE/CSc/IT/9502/Nov'24**  
**(For 2023 batch)**

**Duration: 3Hrs.**

**M.Marks:50**

**SECTION-A**

**Q1. Do as directed any nine of the following.**

**9x1=9**

- a. Full form of EBCDIC is \_\_\_\_\_.
- b. Full form of ASCII IS \_\_\_\_\_.
- c. \_\_\_\_\_ and \_\_\_\_\_ are the universal gates.
- d. What is the radix of an octal number?
- e. Define De Morgan's theorem.
- f. How many select lines are there in a 16:1 multiplexer?
- g. PIPO stands for \_\_\_\_\_.
- h. LED stands for \_\_\_\_\_.
- i. Race around condition can be avoided by using master slave JK flip flop. (T/F)
- j. A flip flop is a memory element. (T/F)
- k. A half adder adds \_\_\_\_\_ bits.
- l. 1's complement of 110101 is \_\_\_\_\_.

**SECTION-B**

**Q2. Attempt any five questions.**

**5x4=20**

- i. Differentiate between analog and digital signals.
- ii. Draw and explain the circuit of half adder.
- iii. Define SSI, MSI, LSI, VLSI and ULSI.
- iv. Draw symbol and truth table of NOT, AND, NOR gate.
- v. Draw logic circuit of 4:1 multiplexer and explain its working.
- vi. What are shift registers? Give its types.
- vii. Write down the applications of A/D and D/A converters.

**SECTION-C**

**Q3. Attempt any three questions.**

**3x7=21**

- a. Discuss symbol and truth table of OR, AND, NOT, NAND, NOR gates.
- b. What is a latch? Explain working principle of JK master /slave flip flop and draw its truth table
- c. Explain the working of 3-bit asynchronous counter.
- d. Write a short note on i) Decoder ii) Seven Segment display
- e. Minimize and realize following logic functions using K-map  
f (A, B, C,D) =  $\sum m (0,1,2,5,8,9,10)$