

**ANALOG ELECTRONICS**  
**3<sup>rd</sup> Exam/Elect/6521/Nov'24**  
**(For 2018 Batch Onwards)**

**Duration: 3Hrs.**

**M.Marks:75**

**SECTION-A**

**Q1. Do as directed.**

**15x1=15**

- a. The difference between the energies of conduction band and valence band is called \_\_\_\_\_
- b. Which are the majority charge carriers in n-type semiconductor?
- c. Name any two active components.
- d. A crystal diode acts as an \_\_\_\_\_ switch.
- e. What is an ideal diode?
- f. What is ripple factor?
- g. Zener diode is made to operate in \_\_\_\_\_ region.
- h. Which are the three terminals of BJT?
- i. In active region, the input junction of a transistor is \_\_\_\_\_ biased and the output junction is \_\_\_\_\_ biased.
- j. What is a thermal runaway of transistor?
- k. For a transistor to work as an amplifier, its operating point should lie in \_\_\_\_\_ region.
- l. The point of intersection of d.c. and a.c. load lines is called \_\_\_\_\_
- m. Which type of coupling is preferred for impedance matching?
- n. MOSFET stands for?
- o. FET is a \_\_\_\_\_ device.

**SECTION-B**

**Q2. Attempt any six questions.**

**6x5=30**

- i. What are intrinsic and extrinsic semiconductors? How we can increase their conductivities?
- ii. Explain the working and V-I characteristics of PN junction diode.
- iii. Explain the circuit and working of pie filter.
- iv. Explain the working of NPN transistor.
- v. Why CE is the most preferred transistor configuration?
- vi. Explain the circuit and working of zener diode as voltage stabilizer.
- vii. What are the difference between BJT and FET?
- viii. Explain the concept of d.c. and a.c. load lines.
- ix. Explain the terms: Frequency response, Decibel gain and Bandwidth.

**SECTION-C**

**Q3. Attempt any three questions.**

**3x10=30**

- a. Explain the circuit and working of centre tap full wave rectifier with advantages & disadvantages.
- b. Draw and explain the input & output characteristics of transistor in Common Emitter configuration in details.
- c. What is multistage amplifier? Explain the circuit and working of RC coupled multistage transistor amplifier with advantages and disadvantages.
- d. Explain the construction, working and characteristics of MOSFET.
- e. i) What is stabilisation? Explain the need of stabilisation of operating point.  
ii) Explain the concept of hybrid parameters of a transistor?