

S. B. Roll. No.....

ELECTRONIC DEVICES AND CIRCUITS
3rd Exam/ECE/6408/Nov'24
(For 2023 Batch)

Duration: 3Hrs.

M.Marks:50

SECTION-A

Q1. Do as directed any nine of the following.

9x1=9

- a. RC Coupled amplifiers are used for amplification of _____.
- b. In multistage amplifier there are two or more stages. (T/F)
- c. In power amplifiers usually _____ coupling is employed.
- d. Distortion is minimum in _____ type of power amplifier.
- e. Complementary PUSH PULL amplifier uses two amplifiers. (T/F)
- f. Oscillators use _____ feedback.
- g. Negative amplifier increases the stability of its voltage gain. (T/F)
- h. Wein ridge oscillator is useful for _____ frequency.
- i. Differentiator circuit is _____ filter.
- j. To generate square wave _____ multivibrator is used.
- k. A 555 timer is 8 pin IC. (T/F)
- l. CMRR Stands for?

SECTION-B

Q2. Attempt any five questions.

5x4=20

- i. Discuss the need for multistage amplifier.
- ii. Differentiate voltage and power amplifiers.
- iii. Write the main features of Emitter Follower Amplifier.
- iv. Describe Barkhausen criterion for oscillations.
- v. Define clipper and clamper circuits.
- vi. How you see 555 timers as monostable multivibrator.
- vii. Write ideal characteristics of an operational amplifier.

SECTION-C

Q3. Attempt any three questions.

3x7=21

- a. Compare RC Coupling, Transformer Coupling and Direct Coupling.
- b. Explain the working of push-pull amplifier.
- c. Discuss the effect of feedback (negative) on gain, distortion and bandwidth of an Amplifier.
- d. Discuss Colpitt Oscillator.
- e. Explain RL circuit as differentiator.